

Answer Sheet: Online Examination

Roll No.:	16010121045	
Course	EEEE	Page No
Date	23/12/21	1

Name of the student:

Pargat Singh Dhanjal


Signature of the student:

Pargat

Q1)

- 1) D) 100 Ohms
- 2) A) low, high & moderate respectively
- 3) A) Forward bias & Forward bias
- 4) C) 0.7V and 0.3V
- 5) D) saturation ~~and~~, cut-off ~~regions~~ and active region.
- 6) B) 12.5 watts
- 7) C) Both Electron and Holes
- 8) D) 25 V and 50 V
- 9) C) out of phase with input voltage and has positive DC shift
- 10) D) 10 V

Q2) i)

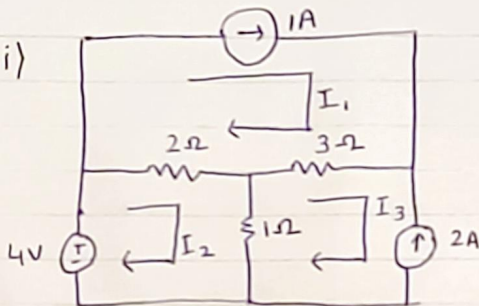

Using Mesh analysis,
There are three mesh

$$\therefore I_1 = 1A \rightarrow \textcircled{1}$$

$$I_3 = -2A \rightarrow \textcircled{2}$$

For mesh $\textcircled{2}$, using KVL

$$+4 - 2(I_2 - I_1) - 1(I_2 - I_3) = 0$$

$$4 - 2I_2 + 2I_1 - I_2 + I_3 = 0$$

$$4 - 2I_2 + 2 - I_2 - 2 = 0 \quad (\text{From } \textcircled{1} \& \textcircled{2})$$

$$-3I_2 = -4$$

$$I_2 = 4/3 \text{ A} \Rightarrow 1.33A$$

\therefore Current through 1Ω resistor = $I_2 - I_3 \Rightarrow 3.33A$

$$\text{Power} = I^2 R = (3.33)^2 \times 1 = \boxed{11.09 \text{ W}}$$

Answer Sheet: Online Examination

Roll No.:	16010121045	
Course	EEEE	Page No
Date	23/12/21	2


Name of the student:

Paugat Singh Dhanjal

Signature of the student: _____

Paugat

Q2) ii)

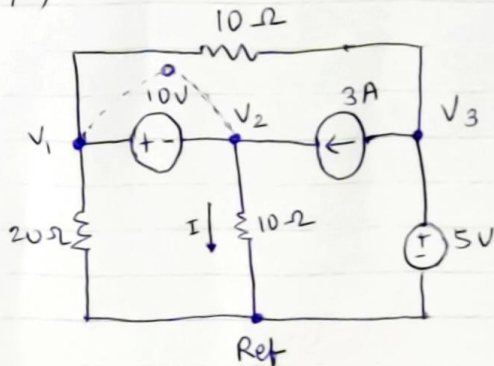

To find current I using Nodal Analysis.

We have 4 nodes, one of them being reference node.

For Node 1,

\therefore There is no resistance between node 1 & 2. It's a supernode using KVL

$$V_1 - 10 - V_2 = 0$$

$$V_1 - V_2 = 10 \rightarrow (1)$$

For supernode, using KCL

$$\therefore \frac{V_1 - V_3}{10} + \frac{V_1}{20} + \frac{V_2}{10} - 3 = 0 \rightarrow (2)$$

$$2V_1 - 2V_3 + V_1 + 2V_2 - 60 = 0$$

$$3V_1 + 2V_2 - 2V_3 - 60 = 0 \rightarrow (2)$$

For node (3), using KCL

~~$\frac{V_3 - V_1}{10} + \frac{V_3 - V_2}{10} - 3 = 0$~~ \therefore There is no load b/w V_3 & Ref

$$\therefore V_3 = 5V \rightarrow (3)$$

From (1), (2) & (3)

$$V_1 = 18, V_2 = 8, V_3 = 5$$

$$\therefore I = \frac{V_2}{R} = \frac{8}{10} = \boxed{0.8A}$$

Answer Sheet: Online Examination

Roll No.:	16010121045	
Course	EEEE	Page No
Date	23/12	3


Name of the student:

Pargat Singh Chanzal

Signature of the student:

Pargat

Q3) i)

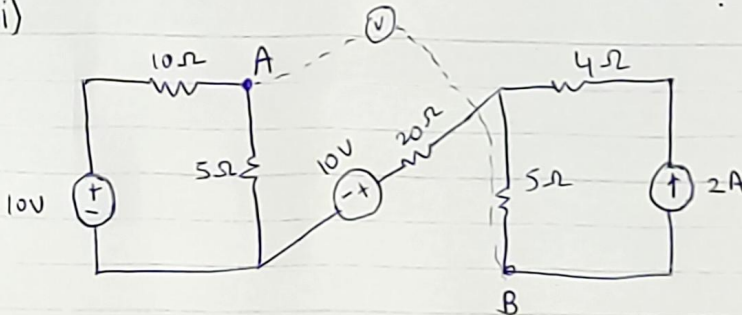

$$I = \frac{10}{5} = 2A$$

Applying Kirchhoff's Voltage Law,

$$V_{AB} - V_{5\Omega} + 10 - V_{20\Omega} - V_{5\Omega} = 0$$

$$V_{AB} - 10 + 10 - (2 \times 5) = 0$$

$$V_{AB} = 10V$$

$$\therefore V_{5\Omega} = 10V$$

$$I_{5\Omega} = 2A$$

(Given)

Q3) ii) P-N junction diode

zener diode

- | | |
|---|--|
| <ul style="list-style-type: none"> • It is uni-directional, i.e. current flows only in one direction through it. • used as a diode for rectification • On reverse biasing, the depletion region is permanently damaged. | <ul style="list-style-type: none"> • It is bi-directional, i.e. current flows in both directions • used for voltage regulation • The reverse bias enables it to allow current bi-directionally. |
|---|--|

Roll No.:	16010121045	
Course		Page No
Date		4.

Name of the student:


Pangat Singh Dhanyal

Signature of the student:

Pangat

Q3) 3.2)

zener-diode as voltage regulator.

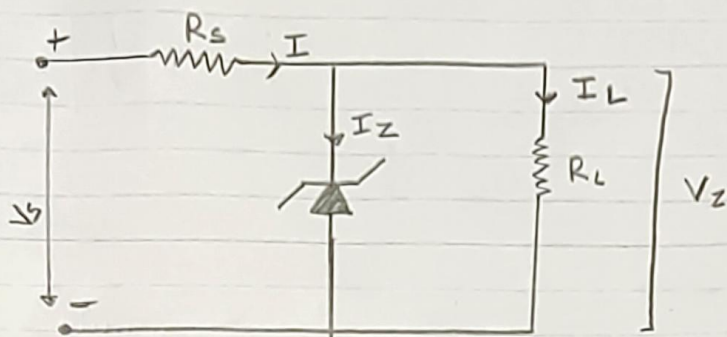

A voltage regulator is an electronic device which regulates or provides a stable, safe DC voltage independent of current (load) and temperature. There is a series resistor connected to the circuit in order to limit the current into the diode. It is connected to the higher potential side of the DC ~~to~~ circuit. It works in such a way that reversed biased can also work in breakdown conditions.

Line Regulation: Here, series & load resistances are fixed, & only the input voltage is changing. Output voltage remains the same as the input voltage is maintained above a minimum ~~to~~ value.

Load Regulation: In this type of regulation, the ~~input~~ ^{input} voltage is fixed & load resistance is variable and the output voltage remains constant as long as the load resistance is maintained above minimum value.